

Quiz 6

60 minutes

Blank Maps for first three problems provided on page 4, but write answers on the page with the problem statement.

1. For the following state table,

| $q_1 q_2$ | $q_1^* q_2^*$ | | z | |
|-----------|---------------|---------|---------|---------|
| | $x = 0$ | $x = 1$ | $x = 0$ | $x = 1$ |
| 0 0 | 0 1 | 1 1 | 0 | 1 |
| 0 1 | 0 0 | 1 0 | 0 | 0 |
| 1 0 | 1 1 | 1 0 | 0 | 1 |
| 1 1 | 0 0 | 1 1 | 0 | 1 |

Show the flip flop input equations and the output equation if the first flip flop is a D flip flop and the second is JK.

$$D_1 =$$

$$J_2 =$$

$$K_2 =$$

$$z =$$

2. For the following state table and state assignment, show the equations and a block diagram for a system using an SR flip flop for q_1 and a T flip flop for q_2 and AND, OR and NOT gates. (Show only one of the solutions for R_1 .)

| q | q * | | z | |
|---|-----|-----|-----|-----|
| | x=0 | x=1 | x=0 | x=1 |
| A | B | C | 1 | 1 |
| B | A | B | 1 | 0 |
| C | B | A | 1 | 0 |

| q | q_1 | q_2 |
|---|-------|-------|
| A | 1 | 0 |
| B | 0 | 1 |
| C | 1 | 1 |

| x | q_1 | q_2 | q_1^* | q_2^* | z |
|---|-------|-------|---------|---------|---|
| 0 | 0 | 0 | | | |
| 0 | 0 | 1 | | | |
| 0 | 1 | 0 | | | |
| 0 | 1 | 1 | | | |
| 1 | 0 | 0 | | | |
| 1 | 0 | 1 | | | |
| 1 | 1 | 0 | | | |
| 1 | 1 | 1 | | | |

$$S_1 =$$

$$R_1 =$$

$$T_2 =$$

$$z =$$

3. Design a counter that goes through the sequence

1 0 7 3 4 2 and repeat

using a D flip flops. Just show the equations.

| A | B | C | A* | B* | C* |
|---|---|---|----|----|----|
| 0 | 0 | 0 | | | |
| 0 | 0 | 1 | | | |
| 0 | 1 | 0 | | | |
| 0 | 1 | 1 | | | |
| 1 | 0 | 0 | | | |
| 1 | 0 | 1 | | | |
| 1 | 1 | 0 | | | |
| 1 | 1 | 1 | | | |

$$D_A =$$

$$D_B =$$

$$D_C =$$

BONUS: Show a state diagram, including what happens if the system begins in state 5 or 6.

For problems 1 to 3

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

| | 0 | 1 |
|----|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

4. Show a state table or a state diagram for a system with one input, x , and one output, z , such that $z = 1$ if and only if the input has been at least three consecutive 1's followed by two 0's. (Full credit for a system with 5 states.)

Example

| | | | | | | | | | | | | | | | | | | |
|-----|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| x | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | | |
| z | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |