

CONTENTS

Preface xvii

CHAPTER 1

Mechanical and Electromagnetic Fundamentals 1

- 1.1** Electric Machines and Power Systems 1
 - Generators* 1
 - Transformers* 3
 - Power Lines* 3
 - Loads* 3
 - Protective Devices* 3
 - The Structure of This Book* 4
- 1.2** A Note on Units and Notation 4
- 1.3** Rotational Motion, Newton's Law, and Power Relationships 5
 - Angular Position θ* 5
 - Angular Velocity ω* 6
 - Angular Acceleration α* 6
 - Torque τ* 7
 - Newton's Law of Rotation* 8
 - Work W* 9
 - Power P* 9
- 1.4** The Magnetic Field 10
 - Production of a Magnetic Field* 11
 - Magnetic Circuits* 13
 - Magnetic Behavior of Ferromagnetic Materials* 24
 - Energy Losses in a Ferromagnetic Core* 29
- 1.5** Faraday's Law—Induced Voltage from a Time-Changing Magnetic Field 31
- 1.6** Production of Induced Force on a Wire 35
- 1.7** Induced Voltage on a Conductor Moving in a Magnetic Field 37

- 1.8** Real, Reactive, and Apparent Power in AC Circuits 39
 - Alternative Forms of the Power Equation* 42
 - Complex Power* 42
 - The Relationships between Impedance Angle, Current Angle, and Power* 43
 - The Power Triangle* 44
- 1.9** Summary 45
- 1.10** Questions 46
- 1.11** Problems 47
- 1.12** References 55

CHAPTER 2

Three-Phase Circuits 56

- 2.1** Generation of Three-Phase Voltages and Currents 56
 - Phase Sequence* 59
- 2.2** Voltages and Currents in a Three-Phase Circuit 60
 - Voltages and Currents in the Wye (Y) Connection* 60
 - Voltages and Currents in the Delta (Δ) Connection* 62
- 2.3** Power Relationships in Three-Phase Circuits 64
 - Three-Phase Power Equations Involving Phase Quantities* 66
 - Three-Phase Power Equations Involving Line Quantities* 67
- 2.4** Analysis of Balanced Three-Phase Systems 68
- 2.5** One-Line Diagrams 75
- 2.6** Using the Power Triangle 75
- 2.7** Questions 78

- 2.8 Problems 78
2.9 References 81

CHAPTER 3

Transformers 82

- 3.1 Why Transformers Are Important to Modern Life 82
- 3.2 Types and Construction of Transformers 83
- 3.3 The Ideal Transformer 85
Power in an Ideal Transformer 87
Impedance Transformation through a Transformer 88
Analysis of Circuits Containing Ideal Transformers 89
- 3.4 Theory of Operation of Real Single-Phase Transformers 93
The Voltage Ratio across a Transformer 95
The Magnetization Current in a Real Transformer 97
The Current Ratio on a Transformer and the Dot Convention 100
- 3.5 The Equivalent Circuit of a Transformer 102
The Exact Equivalent Circuit of a Real Transformer 103
Approximate Equivalent Circuits of a Transformer 105
Determining the Values of Components in the Transformer Model 105
- 3.6 The Per-Unit System 110
- 3.7 Transformer Voltage Regulation and Efficiency 116
The Transformer Phasor Diagram 117
Transformer Efficiency 118
- 3.8 Transformer Taps and Voltage Regulation 125
- 3.9 The Autotransformer 126
Voltage and Current Relationships in an Autotransformer 128
The Apparent Power Rating Advantage of Autotransformers 128

The Internal Impedance of an Autotransformer 132

- 3.10 Three-Phase Transformers 133
Three-Phase Transformer Connections 135
The Per-Unit System for Three-Phase Transformers 141
- 3.11 Transformer Ratings and Related Problems 143
The Voltage and Frequency Ratings of a Transformer 143
The Apparent Power Rating of a Transformer 148
The Problem of Current Inrush 149
The Transformer Nameplate 150
- 3.12 Instrument Transformers 150
- 3.13 Summary 152
- 3.14 Questions 153
- 3.15 Problems 154
- 3.16 References 162

CHAPTER 4

AC Machinery Fundamentals 163

- 4.1 The Rotating Magnetic Field 163
Proof of the Rotating Magnetic Field Concept 166
The Relationship between Electrical Frequency and the Speed of Magnetic Field Rotation 167
Reversing the Direction of Magnetic Field Rotation 170
- 4.2 Magnetomotive Force and Flux Distribution on AC Machines 172
- 4.3 Induced Voltage in AC Machines 175
The Induced Voltage in a Coil on a Two-Pole Stator 176
The Induced Voltage in a Three-Phase Set of Coils 179
The RMS Voltage in a Three-Phase Stator 180
- 4.4 Induced Torque in an AC Machine 181
- 4.5 Winding Insulation in an AC Machine 185
- 4.6 AC Machine Power Flows and Losses 185
The Losses in AC Machines 186

- The Power-Flow Diagram* 187
- 4.7** Voltage Regulation and Speed Regulation 188
- 4.8** Summary 188
- 4.9** Questions 189
- 4.10** Problems 190
- 4.11** References 191
- CHAPTER 5**
- Synchronous Machines** 192
- 5.1** Synchronous Machine Construction 192
- 5.2** The Speed of Rotation of a Synchronous Generator 196
- 5.3** The Internal Generated Voltage of a Synchronous Generator 198
- 5.4** The Equivalent Circuit of a Synchronous Generator 199
- 5.5** The Phasor Diagram of a Synchronous Generator 204
- 5.6** Power and Torque in Synchronous Generators 206
- 5.7** Measuring Synchronous Generator Model Parameters 208
- 5.8** The Synchronous Generator Operating Alone 214
The Effect of Load Changes on a Synchronous Generator Operating Alone 214
Example Problems 217
- 5.9** Synchronous Motors 226
The Equivalent Circuit of a Synchronous Motor 227
The Synchronous Motor from a Magnetic Field Perspective 228
- 5.10** Steady-State Synchronous Motor Operation 229
The Synchronous Motor Torque–Speed Characteristic Curve 229
The Effect of Load Changes on a Synchronous Motor 231
The Effect of Field Current Changes on a Synchronous Motor 235
- The Synchronous Motor and Power-Factor Correction* 240
- 5.11** Starting Synchronous Motors 243
Motor Starting by Using Amortisseur of Damper Windings 245
- 5.12** The Relationship Between Synchronous Generators and Synchronous Motors 249
- 5.13** Synchronous Machine Ratings 250
The Voltage, Speed, and Frequency Ratings 250
Apparent Power and Power-Factor Ratings 251
Short-Time Operation and Service Factor 252
- 5.14** Summary 253
- 5.15** Questions 254
- 5.16** Problems 255
- 5.17** References 264
- CHAPTER 6**
- Parallel Operation of Synchronous Generators** 265
- 6.1** Paralleling Generators 265
The Conditions Required for Paralleling 265
The General Procedure for Paralleling Generators 267
- 6.2** Frequency–Power and Voltage–Reactive Power Characteristics of a Synchronous Generator 269
- 6.3** Operation of Generators in Parallel with Large Power Systems 272
- 6.4** Operation of Generators in Parallel with Other Generators of the Same Size 277
- 6.5** Summary 284
- 6.6** Questions 284
- 6.7** Problems 284
- 6.8** References 287
- CHAPTER 7**
- Induction Motors** 288
- 7.1** Induction Motor Construction 288
- 7.2** Basic Induction Motor Concepts 290

- The Development of Induced Torque in an Induction Motor* 291
- The Concept of Rotor Slip* 293
- The Electric Frequency on the Rotor* 294
- 7.3** The Equivalent Circuit of an Induction Motor 296
- The Transformer Model of an Induction Motor* 296
- The Rotor Circuit Model* 298
- The Final Equivalent Circuit* 299
- 7.4** Power and Torque in an Induction Motor 301
- Losses and the Power-Flow Diagram* 301
- Power and Torque in an Induction Motor* 304
- Separating the Rotor Copper Losses and the Power Converted in an Induction Motor's Equivalent Circuit* 306
- 7.5** Induction Motor Torque–Speed Characteristics 309
- Comments on the Induction Motor Torque–Speed Curve* 312
- Maximum (Pullout) Torque in an Induction Motor* 314
- 7.6** Variations in Induction Motor Torque–Speed Characteristics 321
- Control of Motor Characteristics by Squirrel-Cage Rotor Design* 322
- Deep-Bar and Double-Cage Rotor Designs* 322
- Induction Motor Design Classes* 325
- 7.7** Starting Induction Motors 329
- 7.8** Speed Control of Induction Motors 332
- Induction Motor Speed Control by Pole Changing* 332
- Speed Control by Changing the Line Frequency* 332
- Speed Control by Changing the Line Voltage* 336
- Speed Control by Changing the Rotor Resistance* 336
- 7.9** Determining Circuit Model Parameters 337
- The DC Test for Stator Resistance* 337
- The No-Load Test* 339
- The Locked-Rotor Test* 340
- 7.10** Induction Motor Ratings 345
- 7.11** Summary 347
- 7.12** Questions 347
- 7.13 Problems 348
- 7.14** References 353
- CHAPTER 8**
- DC Motors** 355
- 8.1** The Simplest Possible DC Machine: A Simple Rotating Loop between Curved Pole Faces 356
- The Voltage Induced in a Rotating Loop* 356
- Getting DC Voltage Out of the Rotating Loop* 361
- The Induced Torque in the Rotating Loop* 361
- 8.2** Commutation in a Simple Four-Loop DC Machine 367
- 8.3** Problems with Commutation in Real Machines 372
- Armature Reaction* 373
- L di/dt Voltages* 376
- Solutions to the Problems with Commutation* 378
- 8.4** Power Flow and Losses in DC Machines 382
- The Losses in DC Machines* 383
- The Power-Flow Diagram* 385
- 8.5** Types of DC Motors 386
- 8.6** The Equivalent Circuit of a DC Motor 386
- 8.7** The Magnetization Curve of a DC Machine 389
- 8.8** Separately Excited and Shunt DC Motors 390
- The Terminal Characteristic of a Shunt DC Motor* 390
- Nonlinear Analysis of a Shunt DC Motor* 396

- Speed Control of Shunt DC Motors* 400
- The Effect of an Open Field Circuit* 411
- 8.9** The Permanent-Magnet DC Motor 412
- 8.10** The Series DC Motor 414
 - Induced Torque in a Series DC Motor* 414
 - The Terminal Characteristic of a Series DC Motor* 415
 - Speed Control of Series DC Motors*
- 8.11** The Compounded DC Motor 420
 - The Torque–Speed Characteristic of a Cumulatively Compounded DC Motor* 421
 - The Torque–Speed Characteristic of a Differentially Compounded DC Motor* 423
 - The Nonlinear Analysis of Compounded DC Motors* 423
 - Speed Control in the Cumulatively Compounded DC Motor* 425
- 8.12** DC Motor Starters 425
 - DC Motor Problems on Starting* 426
 - DC Motor Starting Circuits* 430
- 8.13** DC Motor Efficiency Calculations 432
- 8.14** Summary 436
- 8.15** Questions 437
- 8.16** Problems 438
- 8.17** References 445

CHAPTER 9

Transmission Lines 446

- 9.1** Resistance 448
- 9.2** Inductance and Inductive Reactance 450
 - Internal Inductance* 450
 - External Inductance between Two Points Outside of the Line* 452
 - Inductance of a Single-Phase Two-Wire Transmission Line* 454
 - Understanding the Inductance of a Transmission Line* 455
 - Inductive Reactance* 456
- 9.3** Capacitance and Capacitive Reactance 456

- The Electric Field Around a Long, Straight Conductor* 458
- The Capacitance of a Single-Phase Two-Wire Transmission Line* 460
- Understanding the Capacitance of a Transmission Line* 462
- Shunt Capacitive Admittance* 462
- 9.4** Transmission Line Models 464
- 9.5** The Short Transmission Line 466
 - The Phasor Diagram of a Short Transmission Line* 466
- 9.6** Transmission Line Characteristics 467
 - The Effect of Load Changes on a Transmission Line* 467
 - Power Flows in a Transmission Line* 469
 - Transmission Line Efficiency* 472
 - Transmission Line Ratings* 472
 - Transmission Line Limits* 472
 - Example Problem* 473
- 9.7** Two-Port Networks and the ABCD Model 477
- 9.8** The Medium-Length Transmission Line 478
- 9.9** The Long Transmission Line 482
- 9.10** Summary 487
- 9.11** Questions 488
- 9.12** Problems 489
- 9.13** References 491

CHAPTER 10

Power System Representation and Equations 492

- 10.1** One-Line or Single-Line Diagrams 492
- 10.2** Per-Phase, Per-Unit Equivalent Circuits 494
- 10.3** Writing Node Equations for Equivalent Circuits 498
- 10.4** Solving Power System Node Equations with MATLAB 501
- 10.5** Summary 508
- 10.6** Questions 508

- 10.7 Problems 509
- 10.8 References 511

CHAPTER 11

Introduction to Power-Flow Studies 512

- 11.1 Basic Techniques for Power-Flow Studies 513
 - Constructing Y_{bus} for Power-Flow Analysis* 514
 - Power-Flow Analysis Equations* 516
 - A Warning about Network Equation Solutions* 526
 - Speeding Up Network Equation Solutions* 526
- 11.2 Adding Generator Busses to Power-Flow Studies 530
- 11.3 The Information Derived from Power-Flow Studies 537
- 11.4 A Simple Power-Flow Program 538
- 11.5 Additional Features of Power-Flow Programs 549
- 11.6 Summary 549
- 11.7 Questions 550
- 11.8 Problems 550
- 11.9 References 554

CHAPTER 12

Symmetrical Faults 555

- 12.1 Fault Current Transients in Machines 556
 - Fault Transients in Synchronous Motors* 560
 - Fault Transients in Induction Motors* 560
- 12.2 Internal Generated Voltages of Loaded Machines under Transient Conditions 564
 - Internal Generated Voltages of Synchronous Motors* 566
- 12.3 Fault Current Calculations using the Bus Impedance Matrix 568
- 12.4 A Simple Fault Current Analysis Program 575

- 12.5 Comments on Fault Current Calculations 582
- 12.6 Short-Circuit MVA 583
- 12.7 Summary 585
- 12.8 Questions 586
- 12.9 Problems 586
- 12.10 References 590

CHAPTER 13

Unsymmetrical Faults 591

- 13.1 Symmetrical Components 591
 - The a Constant* 592
 - Representing Symmetrical Components with the a Constant* 593
 - Finding the Symmetrical Components of an Unbalanced Three-Phase Voltage* 594
 - Finding the Symmetrical Components of an Unbalanced Three-Phase Current* 595
- 13.2 Calculating Real and Reactive Power from Symmetrical Components 597
- 13.3 Sequence Impedances and Sequence Networks 599
 - Positive-, Negative-, and Zero-Sequence Equivalent Circuits of Generators* 599
 - Positive-, Negative-, and Zero-Sequence Equivalent Circuits of Transmission Lines* 602
 - Zero-Sequence Equivalent Circuits of Y and Δ Connections* 603
 - Positive-, Negative-, and Zero-Sequence Equivalent Circuits of Transformers* 603
 - Building Zero-Sequence Equivalent Circuits* 606
- 13.4 Single Line-To-Ground Fault on an Unloaded Generator 609
- 13.5 Line-To-Line Fault on an Unloaded Generator 614
- 13.6 Double Line-To-Ground Fault on an Unloaded Generator 618
- 13.7 Unsymmetrical Faults on Power Systems 623

- Single Line-to-Ground Faults on a Power System* 625
- Line-to-Line Faults on a Power System* 625
- Double Line-to-Ground Faults on a Power System* 627
- 13.8** Analysis of Unsymmetrical Faults Using the Bus Impedance Matrix 637
- 13.9** Fault Current Analysis Program for Unsymmetrical Faults 641
- 13.10** Summary 643
- 13.11** Questions 646
- 13.12** Problems 646
- 13.13** References 651

APPENDIX **A**
Tables of Constants and Conversion Factors 653

Appendix **B**
Thevenin's and Norton's Theorems 655

APPENDIX **C**
Faults Through and Impedance 657

APPENDIX **D**
Trigonometric Identities 663
Index 665